

# 12 Volt Timer w 2 Circuit Relay Color Coding

## Timer

Purchased at Amazon

Can be set to run from 1 second to up to 1 hour (60 Minutes)

Optimum operation is 12 Volts DC

See Info—all 12 volt timer sheet

I have used the timers in the past wired as shown with the mini relay removed and replaced by two diodes.

I needed to show also how to wire the timers un-changed from the factory.

There are 2 diagrams showing both ways to wire the timer itself.

12 Volt DC Positive Impute.....			12 Volt DC Positive to Timer and Light
12 Volt DC Negative Impute.....			12 Volt DC Negative to timer and light
Button Timer Activation.....			Button Timer Activation to Timer
Button Timer Activation.....			Button Timer Activation to Timer
Button Light Positive.....			Button Light Positive from the Relay
Button Light Negative.....			Button Light Negative from the impute
Hot wire from the power source.....			Hot wire to the relay
Hot Wire to the item to operate.....			Hot Wire from the relay

# Timer Wiring Choices




This is the original Timer purchased as of today and it looks the same.

This timer is wired to activate a 12 Volt DC Relay by activating the timer's attached relay. The timer/relay is a one circuit relay as purchased and can use the same power source to use the



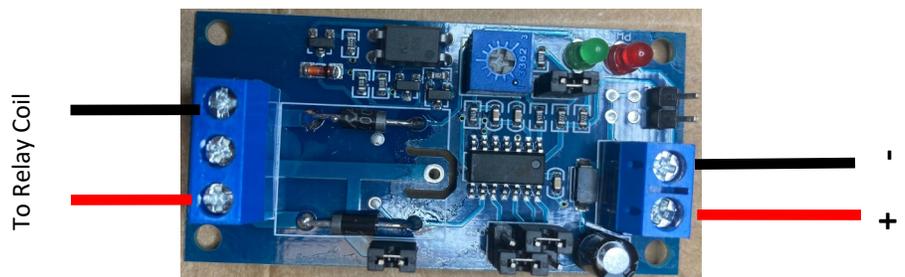This timer is shown with the Relay removed. I have used these timers after removing the relays mostly because some of the attached relays have failed. The timers seem to work




This timer is shown with two diodes replacing the relay.

After I removed the attached relay I then soldered in two diodes across the solder points of the relay. This allows me to wire directly through the timer to activate another relay.

# Basic 12 Volt Timer w 2 Circuit Relay

## New Timer from the Factory

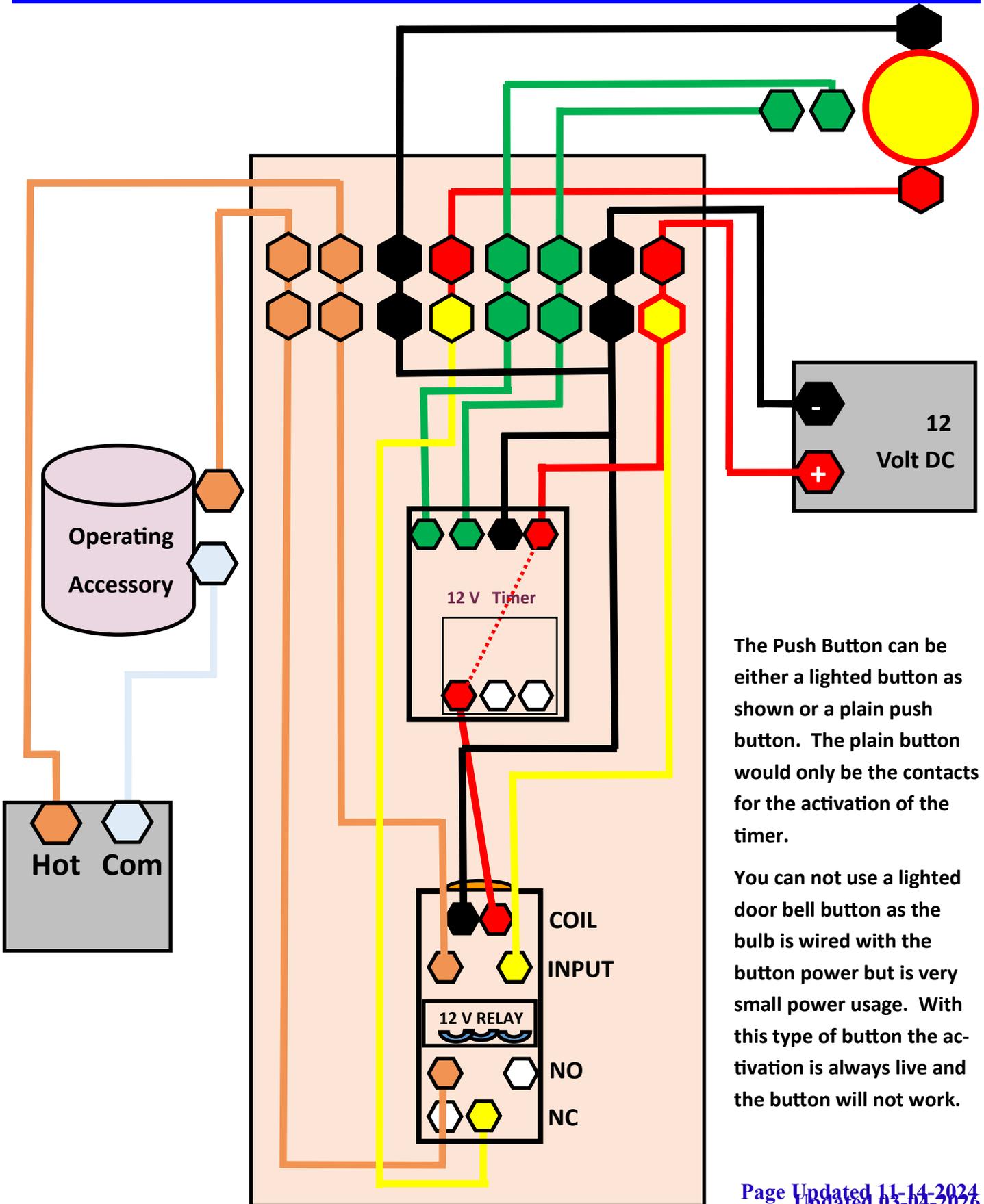


The Push Button can be either a lighted button as shown or a plain push button. The plain button would only be the contacts for the activation of the timer.

You can not use a lighted door bell button as the bulb is wired with the button power but is very small power usage. With this type of button the activation is always live and the button will not work.

# Basic 12 Volt Timer w 2 Circuit Relay

## Timer Relay Removed with added diodes

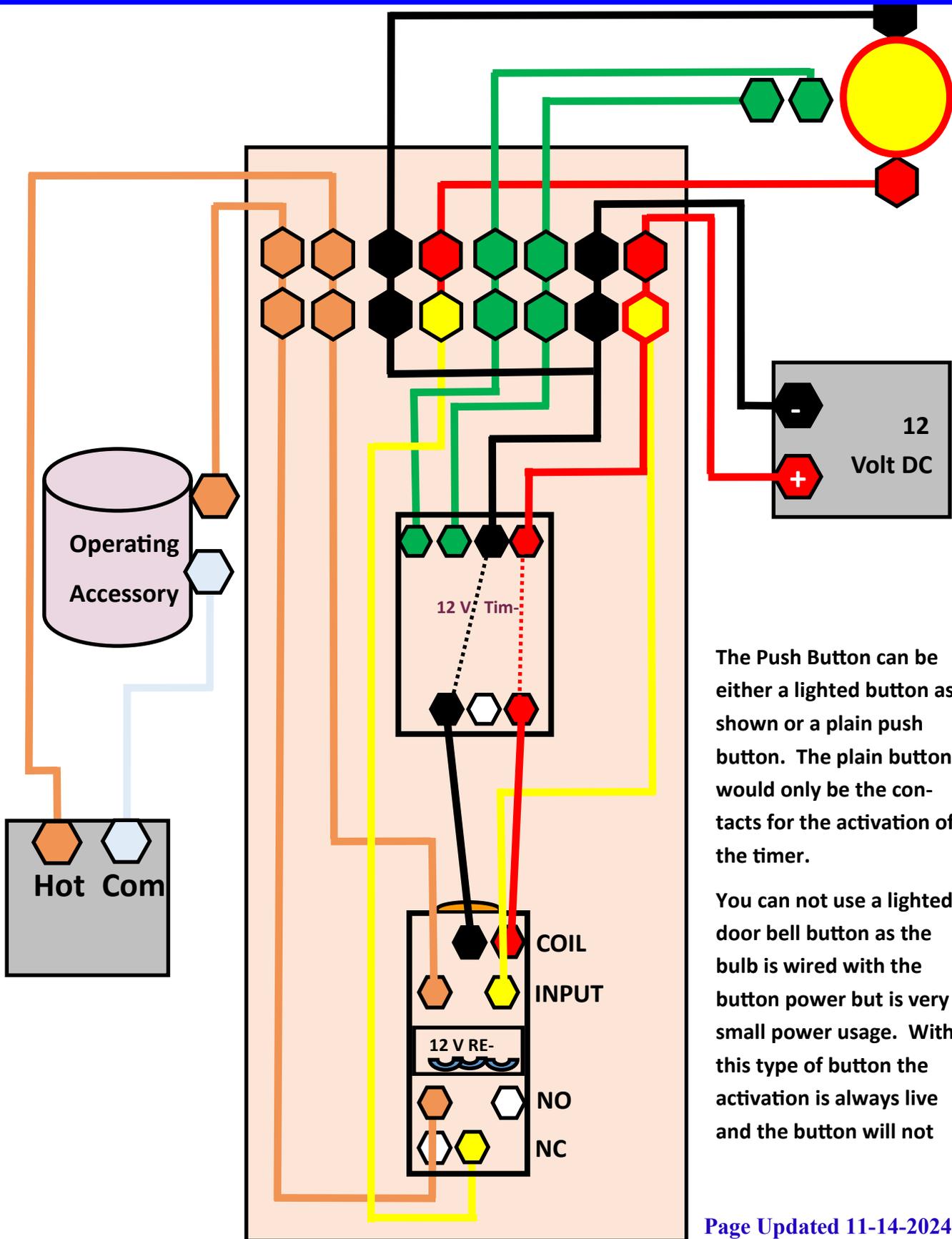


The Push Button can be either a lighted button as shown or a plain push button. The plain button would only be the contacts for the activation of the timer.

You can not use a lighted door bell button as the bulb is wired with the button power but is very small power usage. With this type of button the activation is always live and the button will not

# Chart to set the Timer's Length of Time

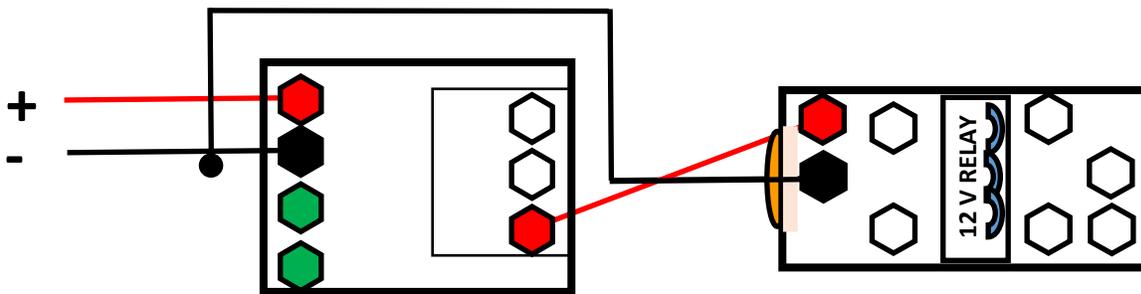**12 Volt DC Power supplies both the timer and the item timed to work with an internal connection.**

- S1 **1 Second to 15 Seconds**
- S2 **1 Second to 60 Seconds**
- S1 **1 Minute to 8 Minutes**
- S2 **6 Minutes to 60 Minutes**



**S5 leave attached to run the relay  
From the timer power 12 V DC**

- S1 = Switch 1
- S2 = Switch 2
- NC = Normally Closed
- NO = Normally Open
- + = Positive DC
- = Negative DC

Activation Wire Pin +



PDF-12 Volt Timer diagram