

## Control 6 small transformers from push buttons

This box will allow the use of up to 6 - 110 volt items to be operated by a Dayton timer to operate all at the same time by pushing a Button be it lighted or not.

You will need the following items

1 House Light Switch

4 Duplex Outlets

You must remove the tab connecting the two hot wire connecting screws. This will make each outlet separate

1 Dayton Timer 110 Volt

3 110 Volt Coil relays (Could use 2 as 6 tabs are unused)

1 Test button no light for inside the box

1 to 4 or more Lighted Buttons to have the guest activate the timer box and the itmes to operate.

1 wall wart 12 v DC transformer to operate the lights in the buttons. (The wall wart is plugged into the outlet marked "LIVE"

The Hot outlet is to allow you to use the 110 outlet as long as the box is plugged into the wall.

All - Wiring E- Button to Switch 6 Circuits - 110 Power Outlets.pub



